



[Visit Suncam.com for more courses](http://www.suncam.com)

Continuing Education Course #062
Switchmode Buck Power Converter
Using Voltage-Mode Control

1. Reasons for using a Buck power converter include:

- a. the output voltage is lower than the supply voltage,
- b. high conversion efficiency is required,
- c. a switch-mode solution is acceptable,
- d. all of the above.

2. Average input and output currents to a Buck converter are nearly equal:

- a. True,
- b. False.

3. The inductor current in a Buck converter is:

- a. constant,
- b. rectangular waveshape,
- c. DC plus a triangular waveshape,
- d. DC plus a rectangular waveshape.

4. The inductor voltage in a Buck converter is:

- a. constant,
- b. rectangular waveshape,
- c. DC plus a triangular waveshape,
- d. DC plus a rectangular waveshape.

5. DC resistance of the inductor in a Buck converter contributes to power loss:

- a. True,
- b. False.

6. Output capacitor ripple voltage in a Buck converter depends on inductor ripple current:

- a. True,
- b. False.

7. Line regulation relates the output voltage changes due to supply changes:

- a. True,
- b. False.

8. Load regulation relates the output voltage changes due to supply changes:

- a. True,
- b. False.

9. The feedforward control in a Buck converter is primarily employed to improve:

- a. line regulation,
- b. load regulation,
- c. both of the above,
- d. none of the above.

10. The inductor/capacitor combination in a Buck converter can introduce an underdamped resonance in the control loop of a Buck converter:

- a. True,
- b. False.

11. The load on a Buck converter can alter the damping of a resonance in the control loop of the Buck converter:

- a. True,
- b. False.

12. The Pole-Zero (PZ) compensator for voltage-mode control uses an integrator pole for:

- a. higher DC gain,
- b. cancellation of resonance induced phase,
- c. PZ compensator bandwidth limitation,
- d. none of the above.

13. The Pole-Zero (PZ) compensator for voltage-mode control uses two zeroes for:

- a. higher DC gain,
- b. cancellation of resonance induced phase,
- c. PZ compensator bandwidth limitation,
- d. none of the above.

14. The Pole-Zero (PZ) compensator for voltage-mode control uses two poles for:

- a. higher DC gain,
- b. cancellation of resonance induced phase,
- c. PZ compensator bandwidth limitation,
- d. none of the above.

15. Switchmode sampling introduces a Zero-Order Hold delay in the feedback loop:

- a. True,
- b. False.

16. Switchmode sampling introduces a Nyquist “notch” in the feedback loop:

- a. True,
- b. False.

17. The pulse-reset sawtooth Pulse-Width Modulator (PWM) can support:

- a. feedforward control,
- b. feedback control,
- c. both feedforward and feedback control,
- d. none of the above.

18. A soft-start reference ramp can be used to:

- a. limit starting current from the supply,
- b. avoid control saturation at startup,
- c. both of the above,
- d. none of the above.

19. A Buck converter with voltage-mode control cannot start with the load applied:
- a. True,
 - b. False.
20. An otherwise stable Buck converter with voltage-mode control can momentarily encounter 100% duty cycle requirements when a transient load is applied suddenly:
- a. True,
 - b. False.
21. An otherwise stable Buck converter with voltage-mode control can momentarily encounter 0% duty cycle requirements when a transient load is removed suddenly:
- a. True,
 - b. False.
22. Required average inductor current changes in a voltage-mode controlled Buck converter are associated with non-zero feedback error voltages:
- a. True,
 - b. False.
23. Sampling a Buck converter with a longer period generally requires larger inductor and capacitor values:
- a. True,
 - b. False.
24. For a synchronously switched Buck converter with a maximum 3.12 μ sec (1-D) switching period, a 3.3V output voltage, and a maximum 200 milli-Ampere peak-to-peak ripple current, the inductor must be:
- a. less than 103 μ H,
 - b. more than 103 μ H,
 - c. none of the above.
25. For a synchronously switched Buck converter with a maximum 312 nsec (1-D) switching period, a 5 milli-Volt ripple voltage, and a maximum 200 milli-Ampere peak-to-peak ripple current, the output capacitor must be,
- a. less than 6.24 μ F,
 - b. more than 6.24 μ F,
 - c. none of the above.

[Purchase this course on Suncam.com](http://Suncam.com)