



[Visit Suncam.com for more courses](http://www.suncam.com)


Continuing Education Course #513  
DC Circuit Fundamentals

1. The voltage drop across a 100 ohm resistor is  $V = 0.2V$ . The current through the resistor is \_\_\_\_\_.  
 a. 0.025 A  
 b. 0.003 A  
 c. 0.002 A  
 d. 0.004 A
2. The current through a 5 kohm resistor is 0.1 m. The voltage drop across the resistor is \_\_\_\_\_.  
 a. 4 V  
 b. 0.1 V  
 c. 3 V  
 d. 0.5 V
3. The voltage drop across a resistor is 0.5 V. The current through the resistor is 0.2 m. The resistance of the resistor is \_\_\_\_\_.  
 a. 2500 ohms  
 b. 250 ohms  
 c. 1470 ohms  
 d. 3000 ohms
4. A 100 ohm resistor has a current of 40 mA running through it. The power dissipated through the resistor is \_\_\_\_\_.  
 a. 0.08 W  
 b. 0.16 W  
 c. 1 W  
 d. 0.32 W
5. The resistor in the problem above is used in a circuit with the same power dissipation. A minimal acceptable power rating for this resistor is \_\_\_\_\_.  
 a. 0.1 W  
 b. 0.08 W  
 c. 0.2 W  
 d. 0.05 W
6. Three resistors are connected in series having values of 150 ohms, 200 ohms, and 350 ohms. The total resistance is \_\_\_\_\_.  
 a. 700 ohms  
 b. 350 ohms  
 c. 200 ohms  
 d. 70 ohms

7. Two resistors are connected in parallel having values of 4.7 kohms and 10 kohms. The total resistance is \_\_\_\_\_.

- a. 1.47 kohms
- b. 5.17 kohms
- c. 4.70 kohms
- d. 3.20 kohms


**Figure A1**

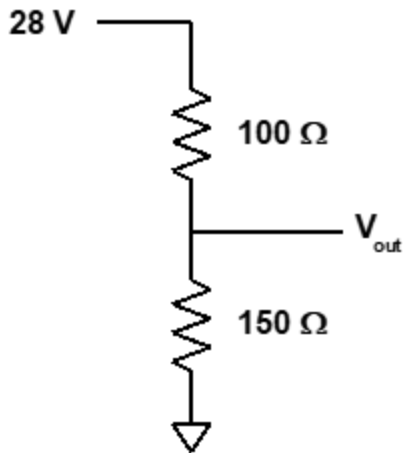

8. The output voltage of the voltage divider shown in Figure A1 is \_\_\_\_\_.

- a. 20.4 V
- b. 16.8 V
- c. 28.0 V
- d. 12.1 V

**Figure A2**

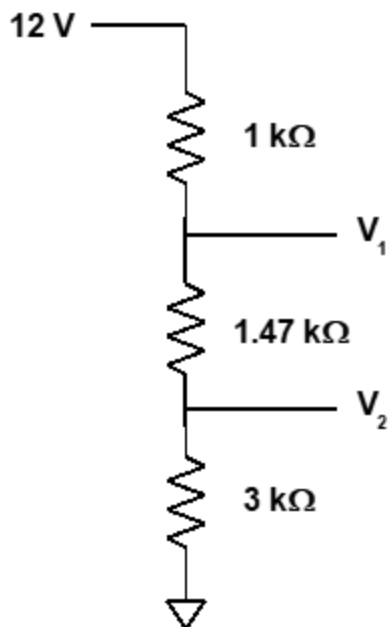

9. The output voltage,  $V_1$ , of the voltage divider shown in Figure A2 is \_\_\_\_\_.


- a. 9.81 V
- b. 8.87 V

- c. 10.3 V
- d. 7.46 V

10. The output voltage,  $V_2$ , of the voltage divider shown in Figure A2 is \_\_\_\_\_.

- a. 5.13 V
- b. 7.24 V
- c. 5.73 V
- d. 6.58 V

**Figure A3**

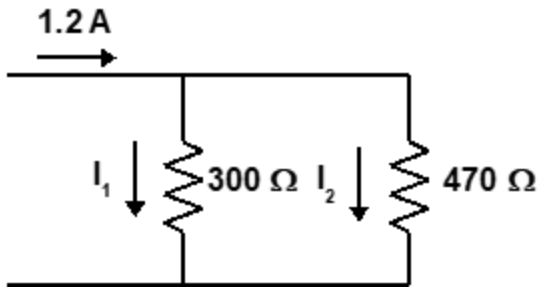


11. The branch current,  $I_1$ , in the current divider shown in Figure A3 is \_\_\_\_\_.

- a. 0.648 A
- b. 0.632 A
- c. 0.732 A
- d. 0.823 A

12. The branch current,  $I_2$ , in the current divider shown in Figure A3 is \_\_\_\_\_.

- a. 0.672 A
- b. 0.468 A
- c. 0.734 A
- d. 0.832 A

**Figure A4**

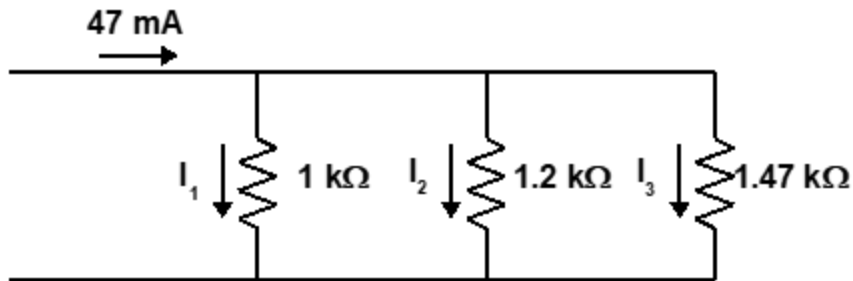

13. The branch current,  $I_1$ , in the current divider shown in Figure A4 is \_\_\_\_\_.

- a. 17.3 mA
- b. 16.8 mA
- c. 19.5 mA
- d. 18.7 mA

14. The branch current,  $I_2$ , in the current divider shown in Figure A4 is \_\_\_\_\_.

- a. 15.6 mA
- b. 17.8 mA

- c. 12.2 mA
- d. 9.87 mA


15. The branch current,  $I_3$ , in the current divider shown in Figure A4 is \_\_\_\_\_.

- a. 13.3 mA
- b. 15.2 mA
- c. 12.7 mA
- d. 21.3 mA

16. Voltage is added when flowing through a source, and subtracted when flowing through a resistor. Conventional current flow is defined as the same direction as \_\_\_\_\_ charges flow.

- a. negative
- b. no
- c. positive
- d. all

**Figure A5**

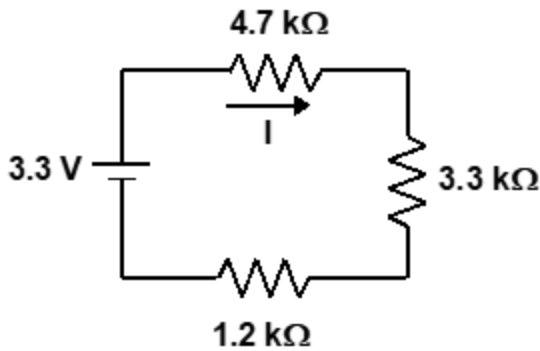

17. For the series circuit shown in Figure A5, the current  $I$  in the circuit is \_\_\_\_\_.

- a. 642  $\mu\text{A}$
- b. 267  $\mu\text{A}$
- c. 481  $\mu\text{A}$
- d. 359  $\mu\text{A}$

18. The voltage drop in the 4.7 kohm resistor in the series circuit shown in Figure A5 is \_\_\_\_\_.

- a. 2.73 V
- b. 1.12 V
- c. 3.72 V
- d. 1.69 V

19. The voltage drop in the 3.3 kohm resistor in the series circuit shown in Figure A5 is \_\_\_\_\_.


- a. 1.18 V
- b. 2.68 V
- c. 0.432 V
- d. 3.12 V

20. The voltage drop in the 1.2 kohm resistor in the series circuit shown in Figure A5 is \_\_\_\_\_.

- a. 0.213 V
- b. 0.430 V


- c. 1.75 V
- d. 0.127 V

**Figure A6**

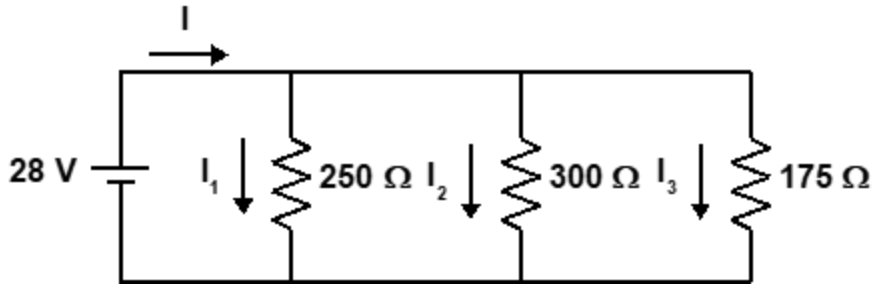

21. For the parallel circuit shown in Figure A6, the current  $I_1$  is \_\_\_\_\_.
- a. 0.212 A
  - b. 0.416 A
  - c. 0.314 A
  - d. 0.112 A
22. For the parallel circuit shown in Figure A6, the current  $I_2$  is \_\_\_\_\_.
- a. 0.127 A
  - b. 0.213 A
  - c. 0.0933 A
  - d. 0.372 A
23. For the parallel circuit shown in Figure A6, the current  $I_3$  is \_\_\_\_\_.
- a. 0.160 A
  - b. 0.153 A
  - c. 0.172 A
  - d. 0.281 A
24. For the parallel circuit in shown in Figure A6, the total current  $I$  is \_\_\_\_\_.
- a. 0.214 A
  - b. 0.576 A
  - c. 0.365 A
  - d. 0.127 A
25. For the parallel circuit shown in Figure A6, the voltage drop across the resistors is \_\_\_\_\_.
- a. 14 V
  - b. 28 V
  - c. 32 V
  - d. 17 V

**Figure A7**

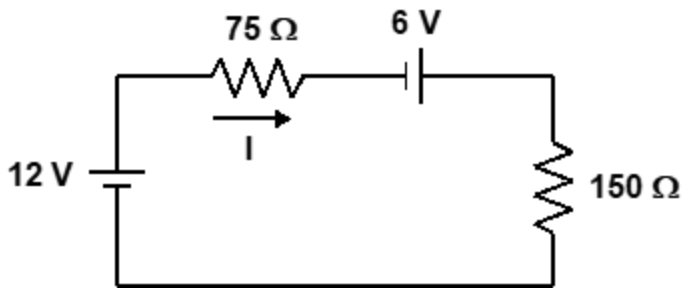

26. In the circuit shown in Figure A7, the current I is \_\_\_\_\_.

- a. 0.12 A
- b. 0.05 A
- c. 0.17 A
- d. 0.08 A


27. In the circuit shown in Figure A7, the voltage drop in the 75 ohm resistor is \_\_\_\_\_.

- a. 6 V
- b. 8 V
- c. 10 V
- d. 12 V

28. In the circuit shown in Figure A7, the voltage drop in the 150 ohm resistor is \_\_\_\_\_.

- a. 6 V
- b. 8 V
- c. 12 V
- d. 10 V

**Figure A8**

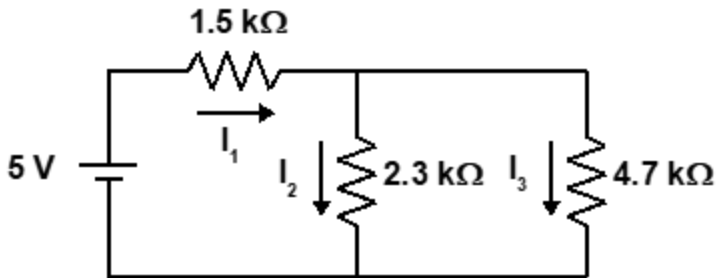

29. In the circuit shown in Figure A8, the current I1 is \_\_\_\_\_.

- a. 2.73 mA
- b. 3.67 mA
- c. 0.157 mA
- d. 1.64 mA


30. In the circuit shown in Figure A8, the current I2 is \_\_\_\_\_.

- a. 2.35 mA
- b. 0.812 mA
- c. 3.72 mA
- d. 1.10 mA

31. In the circuit shown in Figure A8, the current I3 is \_\_\_\_\_.

- a. 0.214 mA
- b. 0.0126 mA
- c. 0.540 mA
- d. 0.725 mA

**Figure A9**

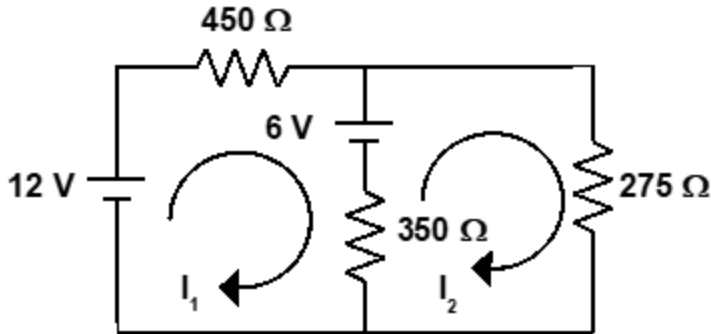


32. In the circuit shown in Figure A9, the mesh current  $I_1$  is \_\_\_\_\_.

- a. 0.0155 A
- b. 0.0286 A
- c. 0.127 A
- d. 0.00861 A

33. In the circuit shown in Figure A9, the mesh current  $I_2$  is \_\_\_\_\_.

- a. 0.0297 A
- b. 0.372 A
- c. 0.218 A
- d. 0.0183 A

**Figure A10**

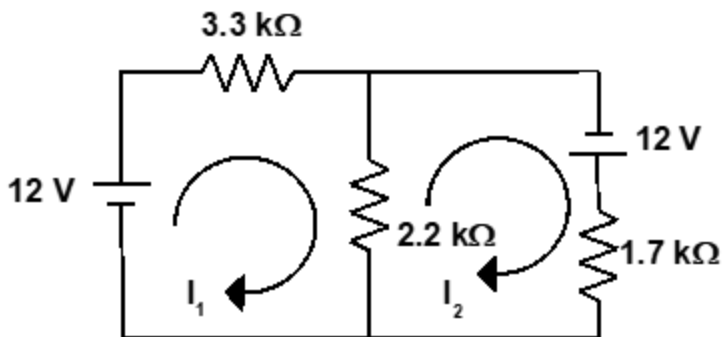

34. In the circuit shown in Figure A10, the mesh current  $I_1$  is \_\_\_\_\_.

- a. 4.41 mA
- b. 2.76 mA
- c. 8.23 mA
- d. 5.91 mA

35. In the circuit shown in Figure A10, the mesh current  $I_2$  is \_\_\_\_\_.

- a. 8.71 mA
- b. 1.23 mA

- c. 5.56 mA
- d. 2.42 mA
36. A series circuit has \_\_\_\_\_ path(s) for current flow.
- a. two
- b. one
- c. multiple
- d. no
37. A parallel circuit has \_\_\_\_\_ path(s) for current flow.
- a. only one
- b. only two
- c. multiple
- d. no
38. A resistor's power rating must be \_\_\_\_\_ than the amount of power being dissipated through it.
- a. greater
- b. less
39. Power dissipation in a resistor \_\_\_\_\_ as resistance increases.
- a. increases
- b. decreases
40. Voltage equals \_\_\_\_\_ times resistance.
- a. voltage
- b. resistance
- c. power
- d. current
41. The equation in the above problem is known as \_\_\_\_\_ Law.
- a. Tesla's
- b. Maxwell's
- c. Ohm's
- d. Faraday's
42. An ohm is defined as the electrical resistance between two points of a conductor when a constant potential difference of \_\_\_\_\_, applied to these points, produces in the conductor a current of 1 amp.
- a. 0 volts
- b. 1 volt
- c. 1000 volts
- d. 2 volts
43. In order to determine the current through a resistor, you must know the resistance as well as the \_\_\_\_\_ across the resistor.
- a. voltage
- b. capacitance
- c. inductance
- d. magnetic field strength
44. Power is measured in \_\_\_\_\_.
- a. watts
- b. ohms

- c. volts
- d. joules

45. In order to find the total resistance in a series circuit, you must \_\_\_\_\_ each resistor value.

- a. subtract
- b. multiply
- c. add
- d. divide

[Purchase this course on Suncam.com](http://Suncam.com)