



[Visit Suncam.com for more courses](http://Suncam.com)

Continuing Education Course #624
Electronics
Course II Fundamental Devices

1. The bandwidth of an amplifier is measured at the 3 dB downpoints. What is the normalized power at the 3 dB downpoint?

- a. 1/2
- b. 1
- c. 3
- d. 6

2. An operational amplifier has a gain of 10^5 . The frequencies at the half-power points are $f_L = 500$ Hz and $f_H = 1000$ Hz. What is most nearly the figure of merit?

- a. 1×10^6 rad/s
- b. 5×10^7 rad/s
- c. 3×10^8 rad/s
- d. 6×10^8 rad/s

3. A low-pass filter has a resonant frequency of 102 Hz. What is the Gain-Bandwidth product for an amplifier with a gain of 10^5 ?

- a. 10^2 Hz
- b. 10^5 Hz
- c. 10^7 Hz
- d. 10^9 Hz


4. What is an operational amplifier's input signal range when the supplying voltage is 12 V and the voltage gain is 10^8 ?

- a. 0.09 μ V
- b. 0.09 nV
- c. 0.12 μ V
- d. 0.12 nV

5. What is the common mode voltage for an input signal range of 9×10^{-8} ?

- a. 0.045 μ V
- b. 0.045 nV
- c. 0.065 μ V
- d. 0.065 nV

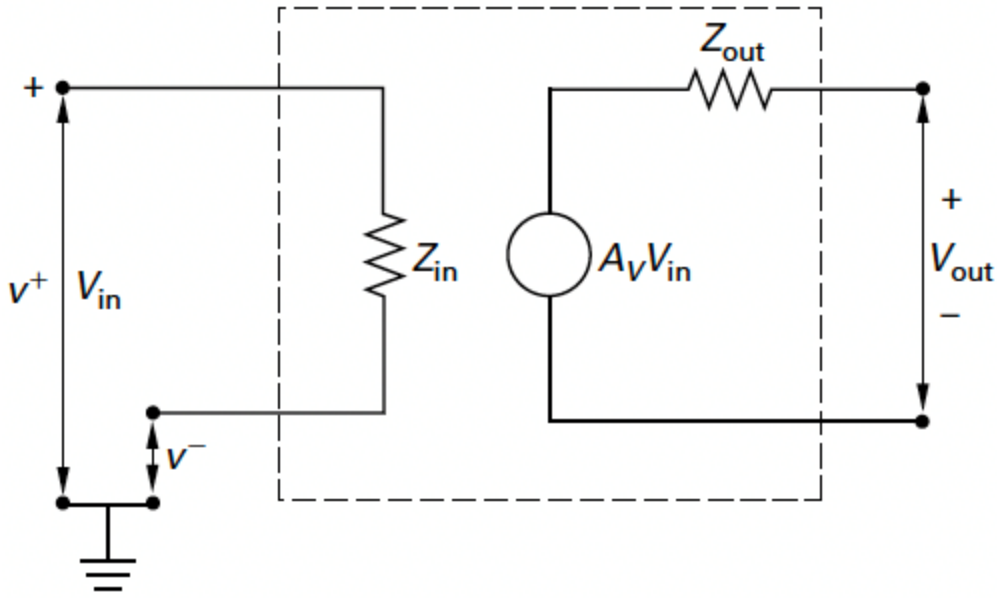6. What equivalent circuit is shown below?



- a. Common Collector Buffer
- b. Common Emitter Follower
- c. Operational Amplifier
- d. Transistor Amplifier

7. The input impedance of an op amp is $10^6 \Omega$. The feedback is used to keep the voltage difference between the input terminals at $0.12 \mu V$.

What is the value of the input current?

- a. 0.12 pA
- b. 1.2 pA
- c. 12 pA
- d. 120 pA


8. Which of the following is NOT a property of an ideal op amp?

- a. $A_V \approx 10^{12}$
- b. $BW = \infty$
- c. $Z_{in} = \infty$
- d. $Z_{out} = 0$

9. Because of the assumptions made for an ideal op amp, the current in to each input is _____.


- a. depends on the feedback
- b. grounded
- c. small
- d. zero

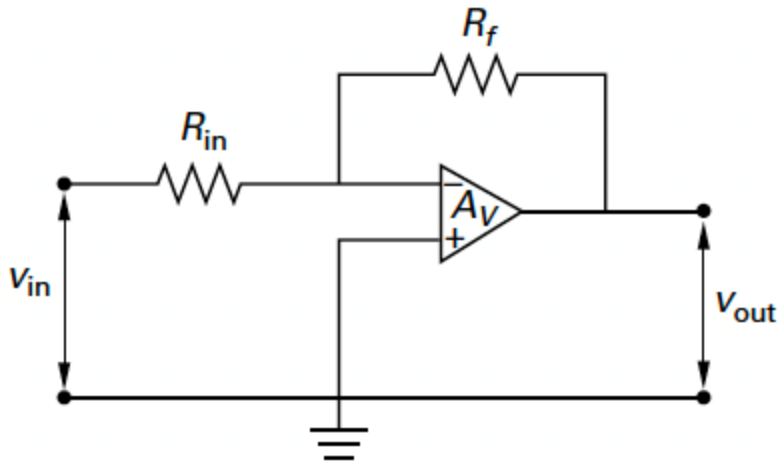10. Consider the circuit shown. The feedback resistance is $10 \text{ k}\Omega$, and the input resistance is 100Ω . If the op amp gain is 10^5 , what is the gain of the circuit? [Use ideal op amp assumptions.]




- a. -100
- b. -90
- c. 100
- d. 10^5

11. What type of amplifier is shown?

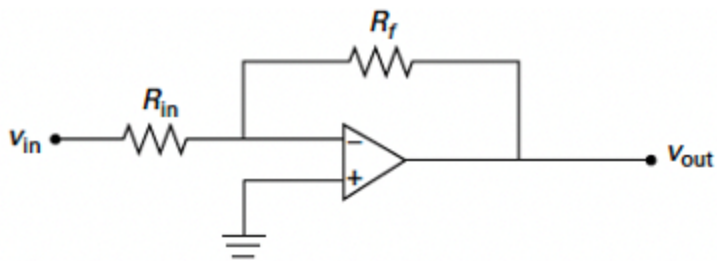


- a. feedback
- b. integrator
- c. inverting
- d. summing

12. What type of amplifier is shown?

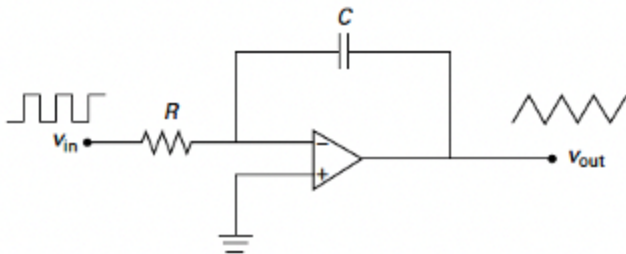


- a. feedback
- b. integrator
- c. inverting
- d. summing

13. What type of amplifier is shown?

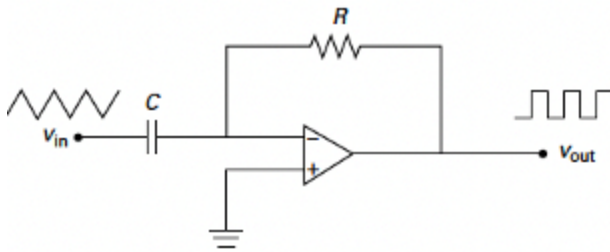

- a. differentiator
- b. integrator
- c. inverting
- d. summing

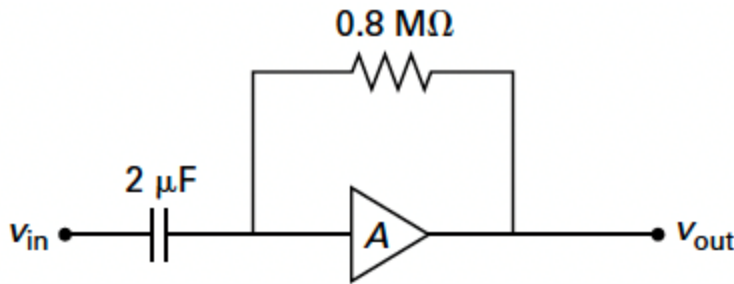14. In the circuit shown, if v_{in} is $\sin 30t$, what is v_{out} ?



Assume the op amp is ideal and has infinite gain.


- a. $1.6 \sin 30t$
- b. $1.6 \cos 30t$
- c. $-48 \cos 30t$
- d. $-48 \sin 30t$

15. An operational amplifier has an input resistance of $10^5 \Omega$ and a bandwidth of 1000 Hz, and is at a room temperature of 300K. Hint: Start with the SNR equation; then use the noise power equation.





If 10 dB above the noise is required for proper operation, what is the required signal power?

- a. $0.10 \mu\text{V}$
- b. $2.0 \mu\text{V}$
- c. $4.0 \mu\text{V}$
- d. $16 \mu\text{V}$


16. Consider the circuit shown.

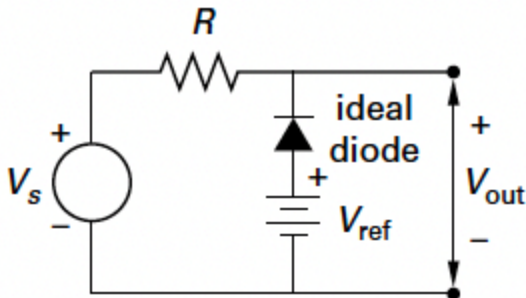

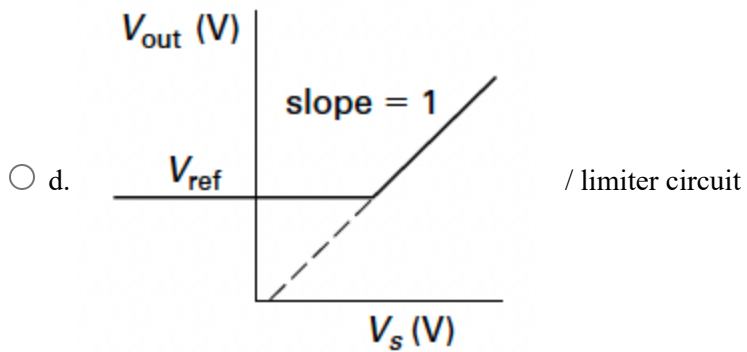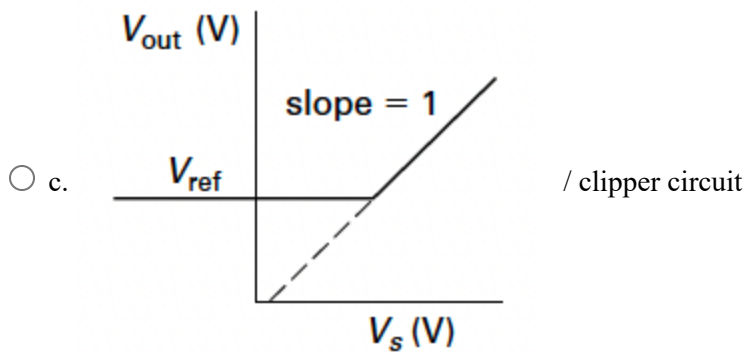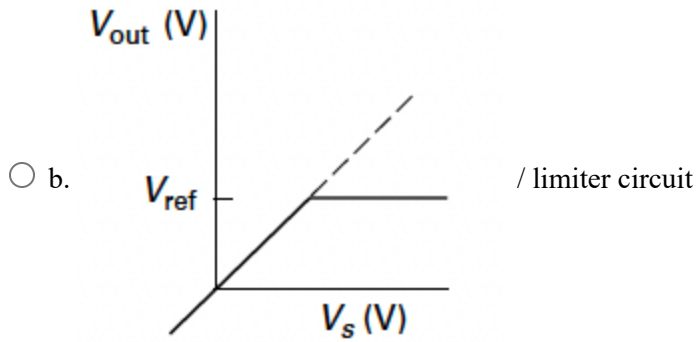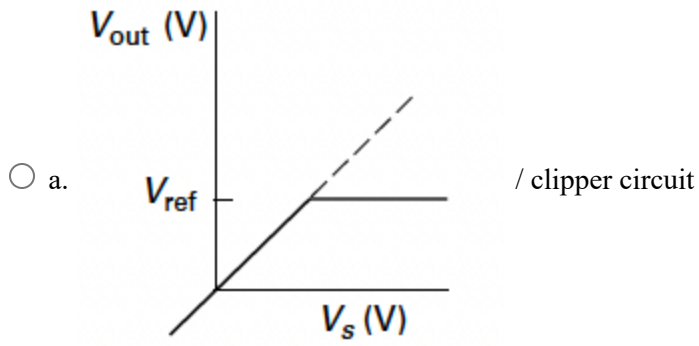What is the output of the circuit? What is the name of the circuit?



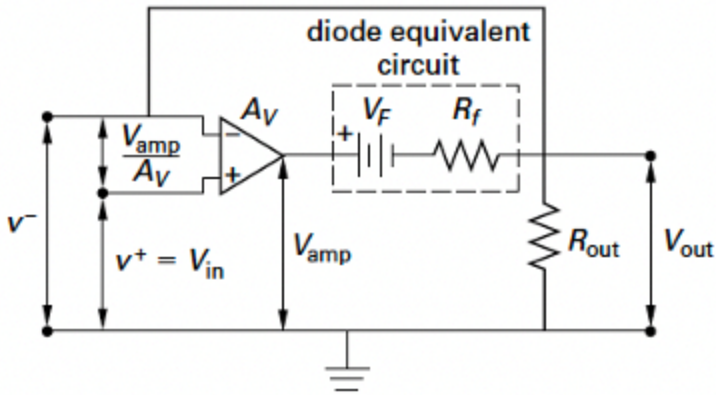17. Consider the precision diode shown with a 9 V power supply and a voltage gain of 10^7 .




What is the maximum voltage difference that can be amplified without distortion or saturation?
Hint: Use the constraint equation.

- a. $0.6 \mu\text{V}$
- b. $0.9 \mu\text{V}$
- c. $6 \mu\text{V}$
- d. 6V

18. A zener diode is meant to operate in the _____ region.

- a. avalanche
- b. breakdown
- c. forward region
- d. forward biased

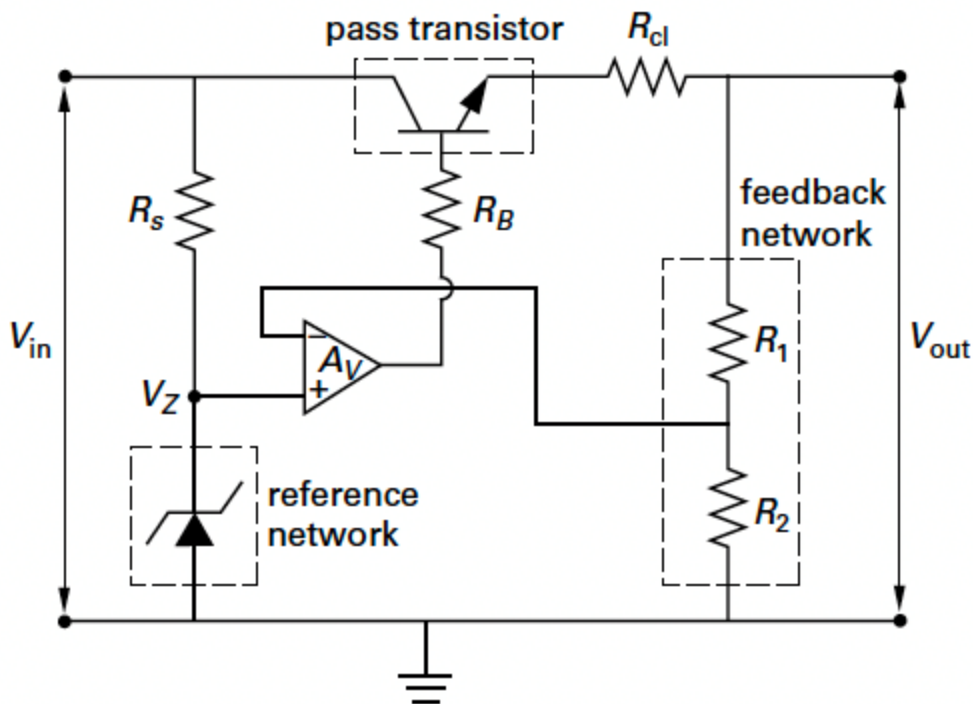19. Consider the regulator circuit shown.




What formula represents the input to the op amp?

- a. V_Z
- b. $-\delta V_{out}$

- c. δ
- d. $V_Z - \delta V_{out}$

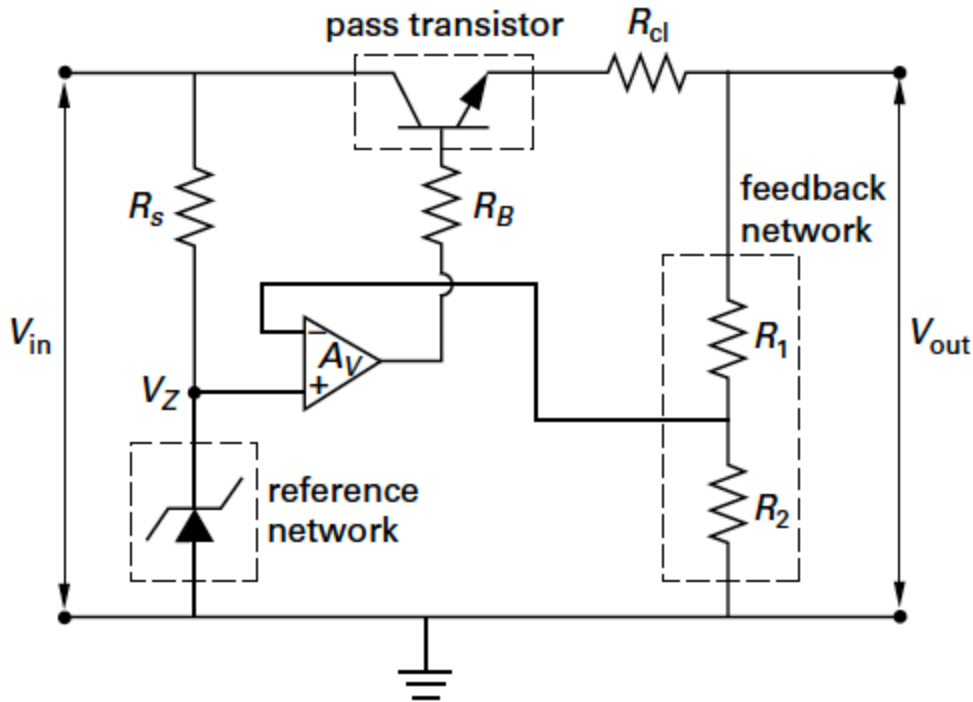20. Consider the regulator circuit shown.



The pass transistor is meant to provide a _____ gain.

- a. current
- b. isolation
- c. resistance
- d. voltage

[Purchase this course on Suncam.com](http://Suncam.com)